

Review 3 Questions.

① Explain the basic operation of a bistable element.

⇒ Bistable elements are used as binary memory cells to store a logic '0' or '1' state.

It is a type of sequential circuit that can hold its state until a new input signal is received, causing the state to change.


It is also called as "one bit memory cell".

The bistable element is a digital circuit with two inputs and one output that has two stable states.

State 1: $Q = 0$ & $\bar{Q} = 1$

State 2: $Q = 1$ & $\bar{Q} = 0$

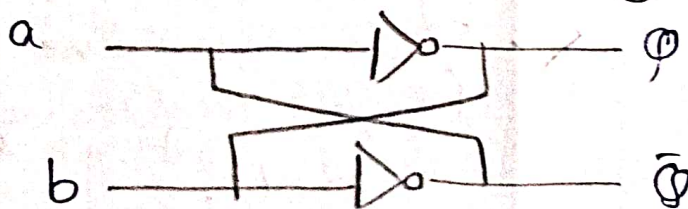The basic bistable element is formed by cross-coupling two NOT gates.



When power on, $a = 0$, $b = 1$ then the output $Q = 1$, $\bar{Q} = 0$ stable state '1'.

When power on, $a = 1$, $b = 0$, then the output $Q = 0$, $\bar{Q} = 1$ stable state '0'.

JK Flip flop vs Latch JK Flip flop?

③ Write the difference between latch & Flip flop.

⇒

Latch

① Latches do not require clock signal.

② A latch is an asynchronous device

③ Latches are transparent devices i.e., they are enabled, the output changes immediately if the input changes

④ A latch is a level sensitive device.

(Level triggering is involved).

⑤ The operation of a latch is faster as they do not have to wait for clock signal.

Flip Flop

Flip-flops have clock signal.


A flip-flop is a synchronous device.

A transition from low to high or high to low of the clock signal will cause the flip flop to either change its output or retain it depending on the input signal.

A flipflop is an edge sensitive device (Edge triggering is involved).

Flip flop are comparatively slower than latches due to clock signal.

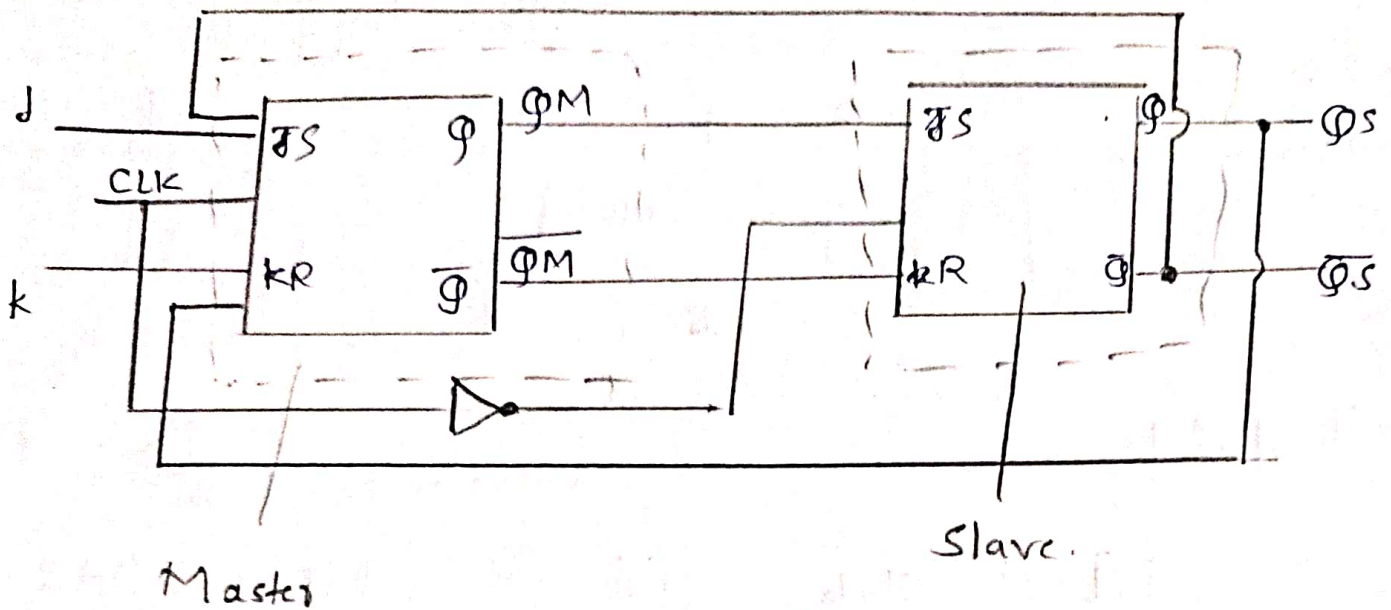④ How do you overcome the limitations of JK Flip flop using Master slave JK Flip flop?



Truth table.

J	K	$Q(t)$	$Q(t+1)$
0	0	$Q(t)$	NC
0	1	0	Reset
1	0	1	Set
1	1	$Q(t)$	Toggle.

Characteristic table

J	K	$Q(t)$	$Q(t+1)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Characteristic equation

J \ K	0	1
0	0	1
1	0	1

$\overline{K}Q(t)$

J \ K	0	1
0	0	0
1	1	0

$J\overline{Q}(t)$


$$Q(t+1) = J\overline{Q}(t) + \overline{K}Q(t)$$

Excitation table


$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

⑤ Derive characteristic equation for JK flip flop

⇒ Block diagram

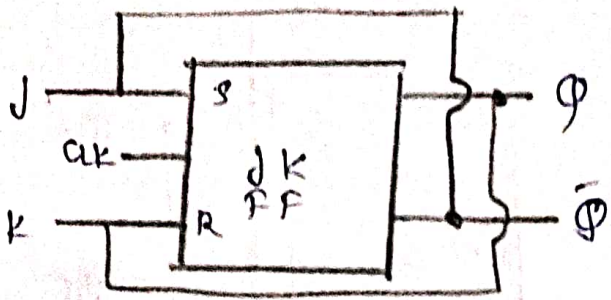

Logic diagram

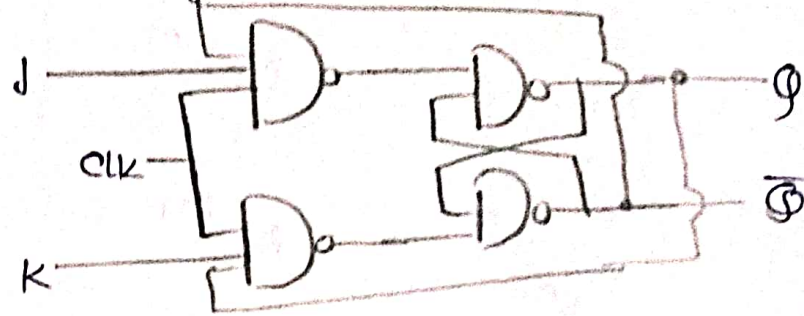

Truth table

J	K	$Q(t+1)$	State
0	0	$Q(t)$	NC
0	1	0	Reset
1	0	1	Set
1	1	$\overline{Q(t)}$	Toggle

Characteristic table

J	K	$Q(t)$	$Q(t+1)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	0	0

Characteristic equation

JK	$Q(t)$		
	0	1	
00	00	1	$\overline{K} Q(t)$
01	02	03	
11	16	07	$J \overline{Q(t)}$
10	14	15	

$$\boxed{Q(t+1) = J \overline{Q(t)} + \overline{K} Q(t)}$$