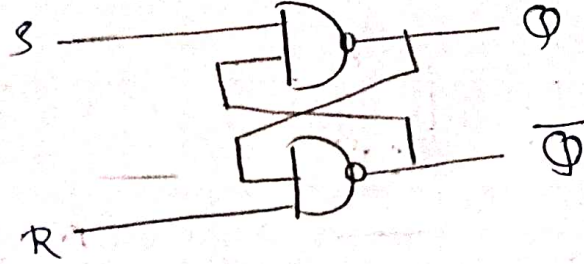


# SR Latch.

Block diagram



Logic diagram



Truth table.

S	R	Q(t+1)	State
0	0	Q(t)	forbidden
0	1	1	Set
1	0	0	Reset
1	1	Q(t)	NC

→ Both o/p remains same

→ stays at previous state.

Characteristic table.

S	R	Q(t)	Q(t+1)
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

} Forbidden state


} Set State

} Reset State

} No change state.

① SR ff.


Truth table

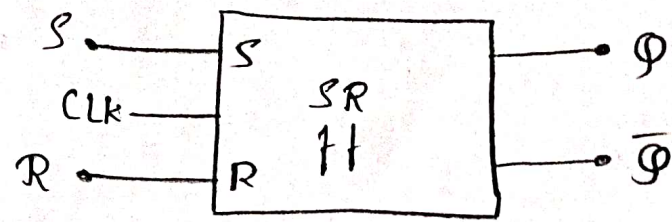

Block diagram.

CLK	S	R	$Q(t+1)$	State
0	x	x	$Q(t)$	previous state.
1	0	0	$Q(t)$	NC
1	0	1	0	Reset
1	1	0	1	Set
1	1	1	x	Forbidden

Logic Circuit diagram

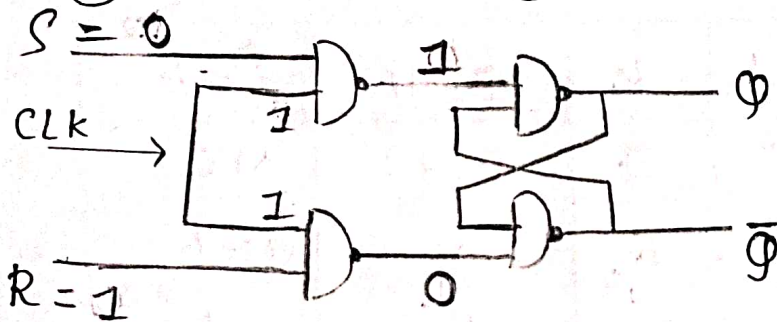

Characteristics table for SR ff.

S	R	$Q(t)$	$Q(t+1)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	x
1	1	1	x

Characteristic Eqn.

SR	$Q(t)$		$\overline{R}Q(t)$
	0	1	
00	0	1	1
01	0	0	
11	x	x	S
10	1	1	


$$Q(t+1) = S + \overline{R}Q(t)$$




# Excitation table

$Q(t)$	$Q(t+1)$	$S$	$R$
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0


## S R - Waveform (Level Triggered).

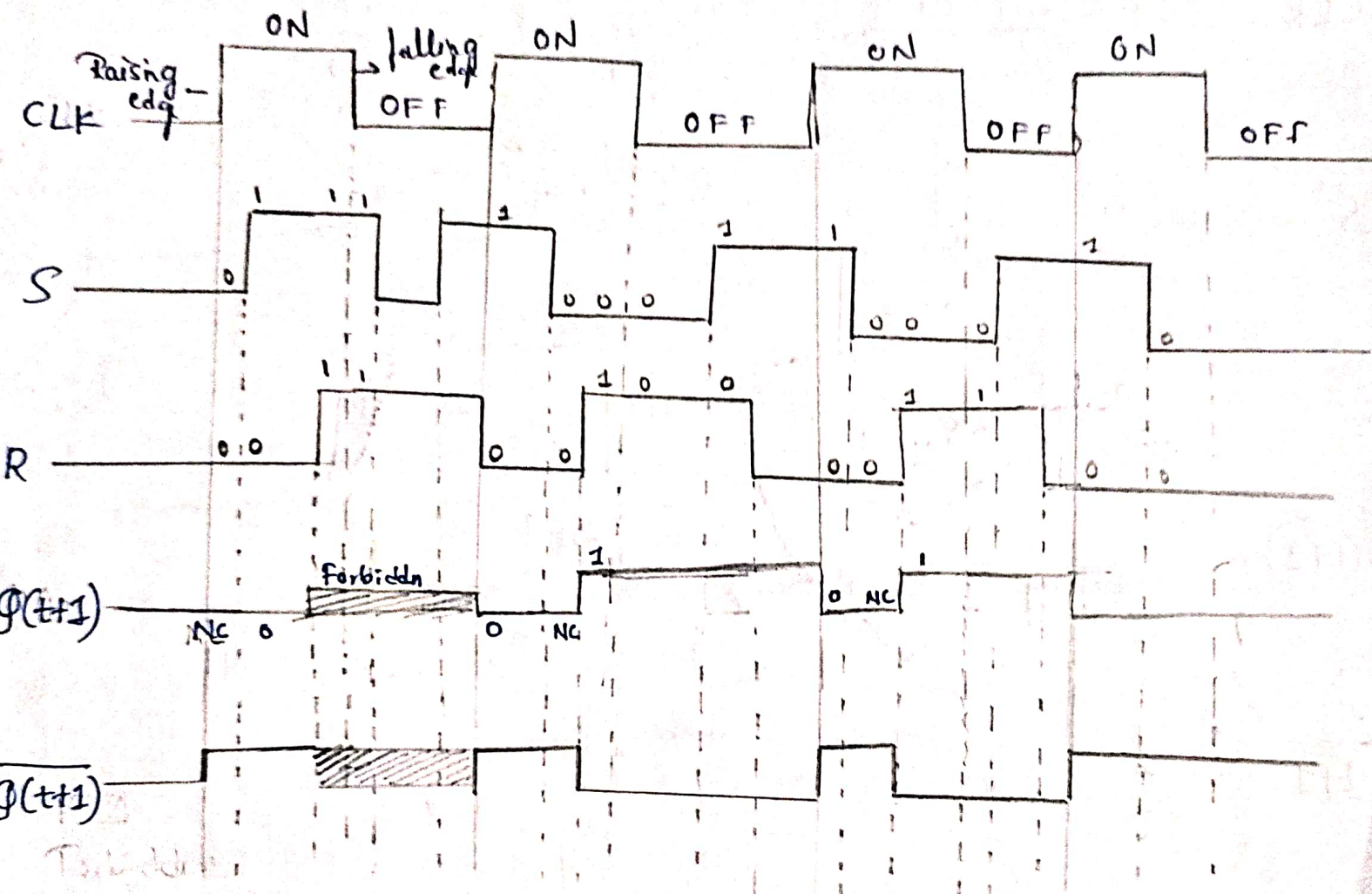



 forbidden.



## S R Waveform (Edge Triggered)

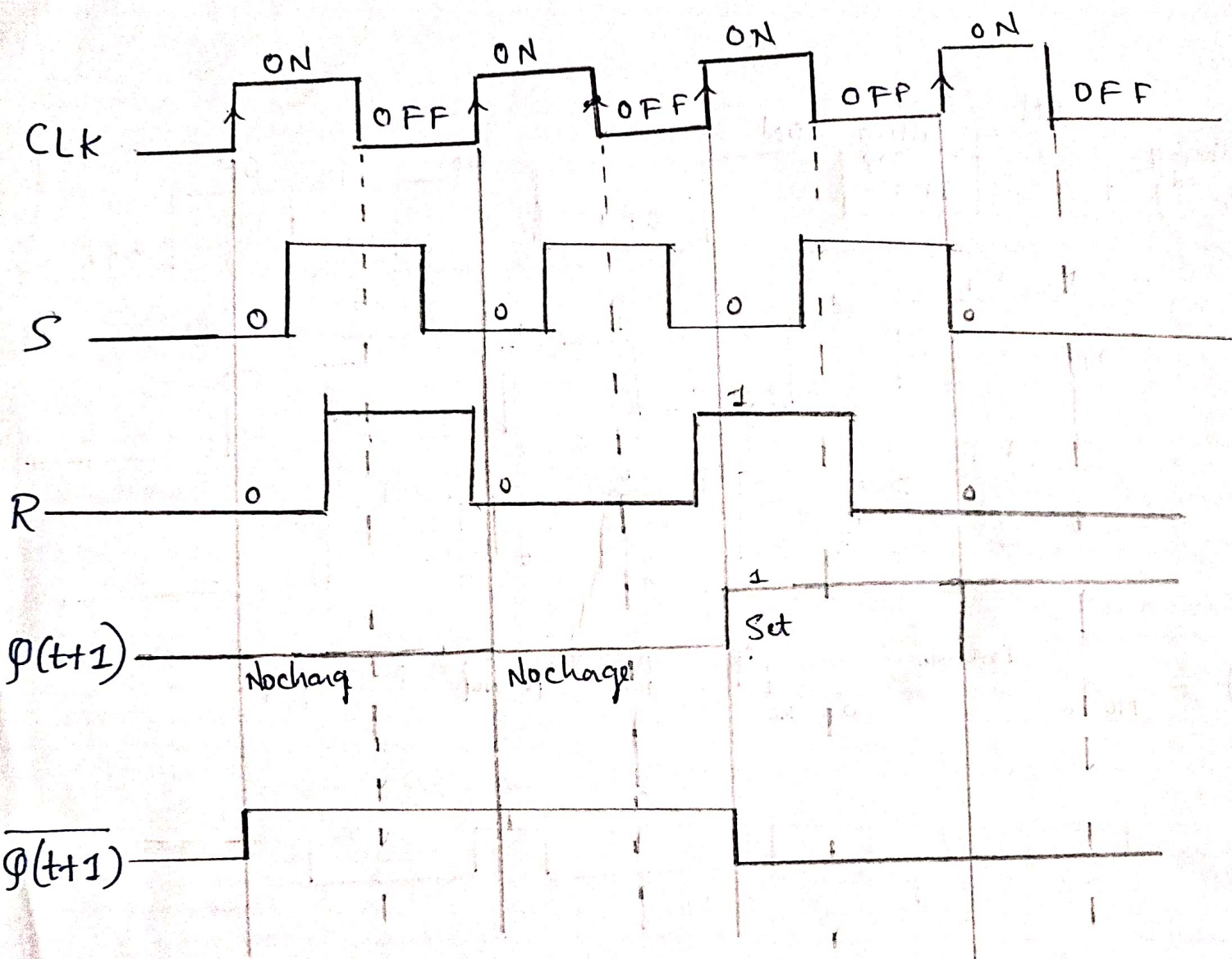

## JK flip flop.

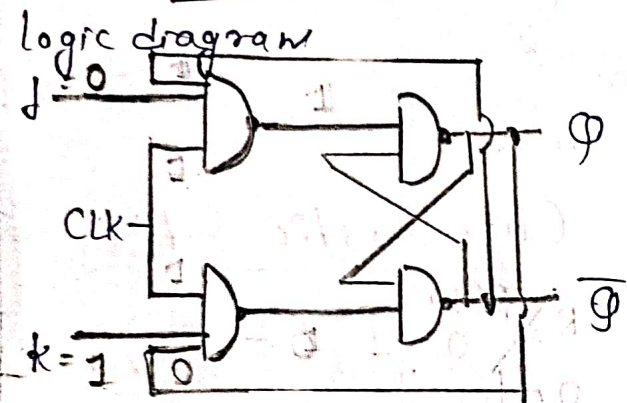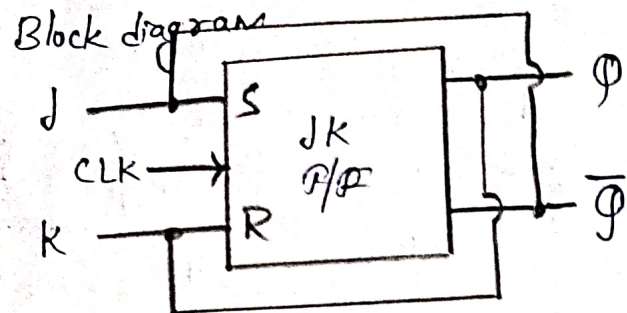

Truth table.

J	K	$Q(t+1)$	State
0	0	$Q(t)$	NC
0	1	0	Reset
1	0	1	Set
1	1	$\overline{Q(t)}$	Toggle

Characteristic table.

J	K	$Q(t)$	$Q(t+1)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Characteristic equation.

J \ K	0	1
0	0	1
1	0	1
1	1	0


$$Q(t+1) = J\overline{Q(t)} + \overline{K}Q(t)$$




## Excitation table.

$Q(t)$	$Q(t+1)$	$J$	$K$
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

## Waveforms.

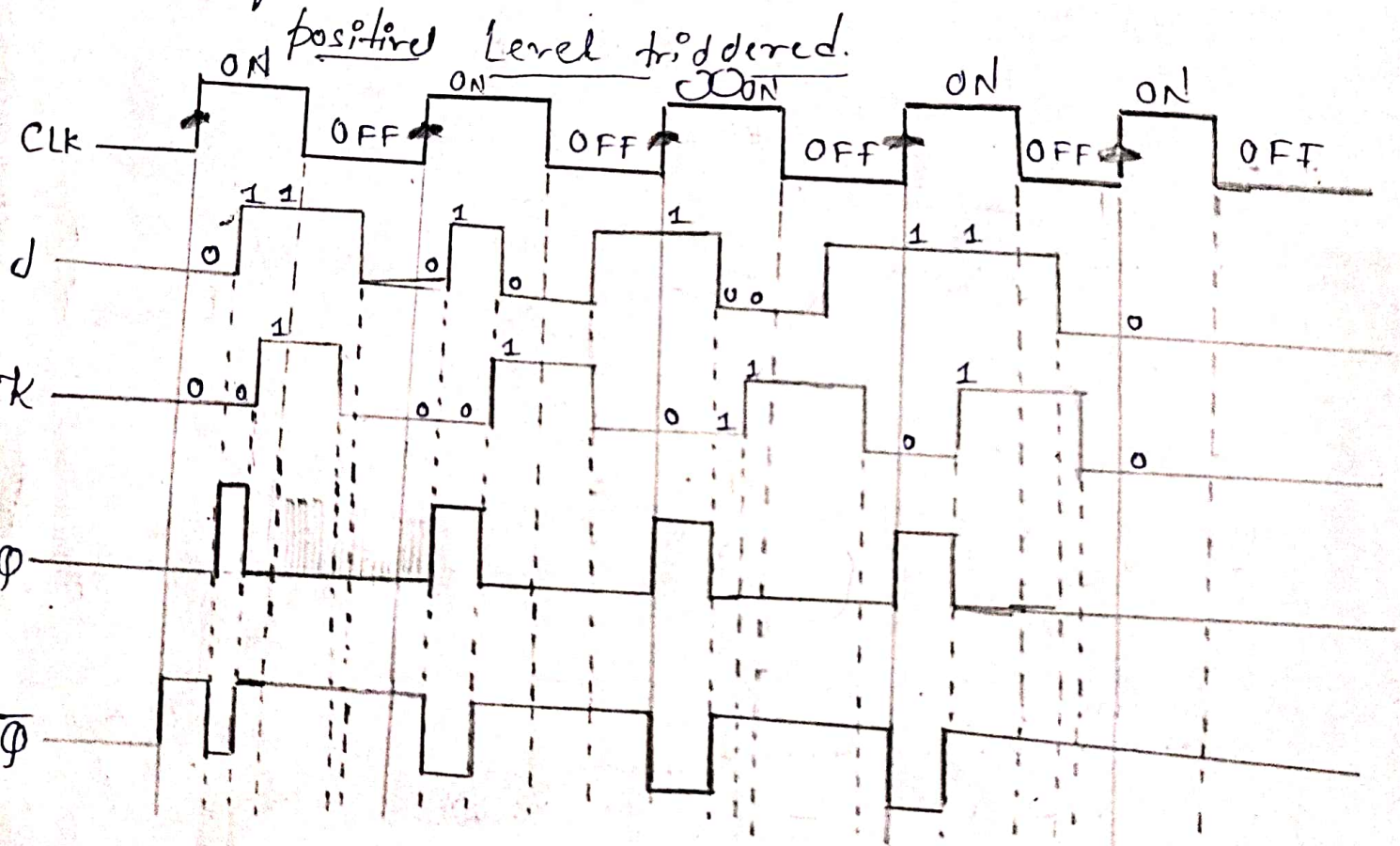


## positive edge triggered

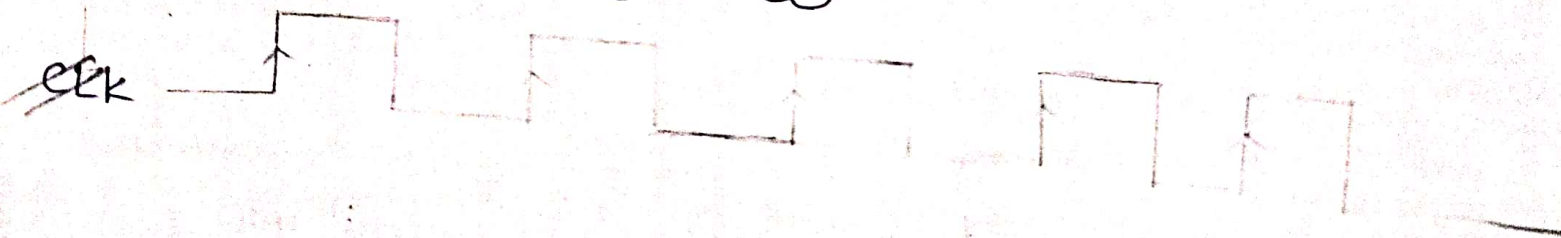





Negative level triggered.

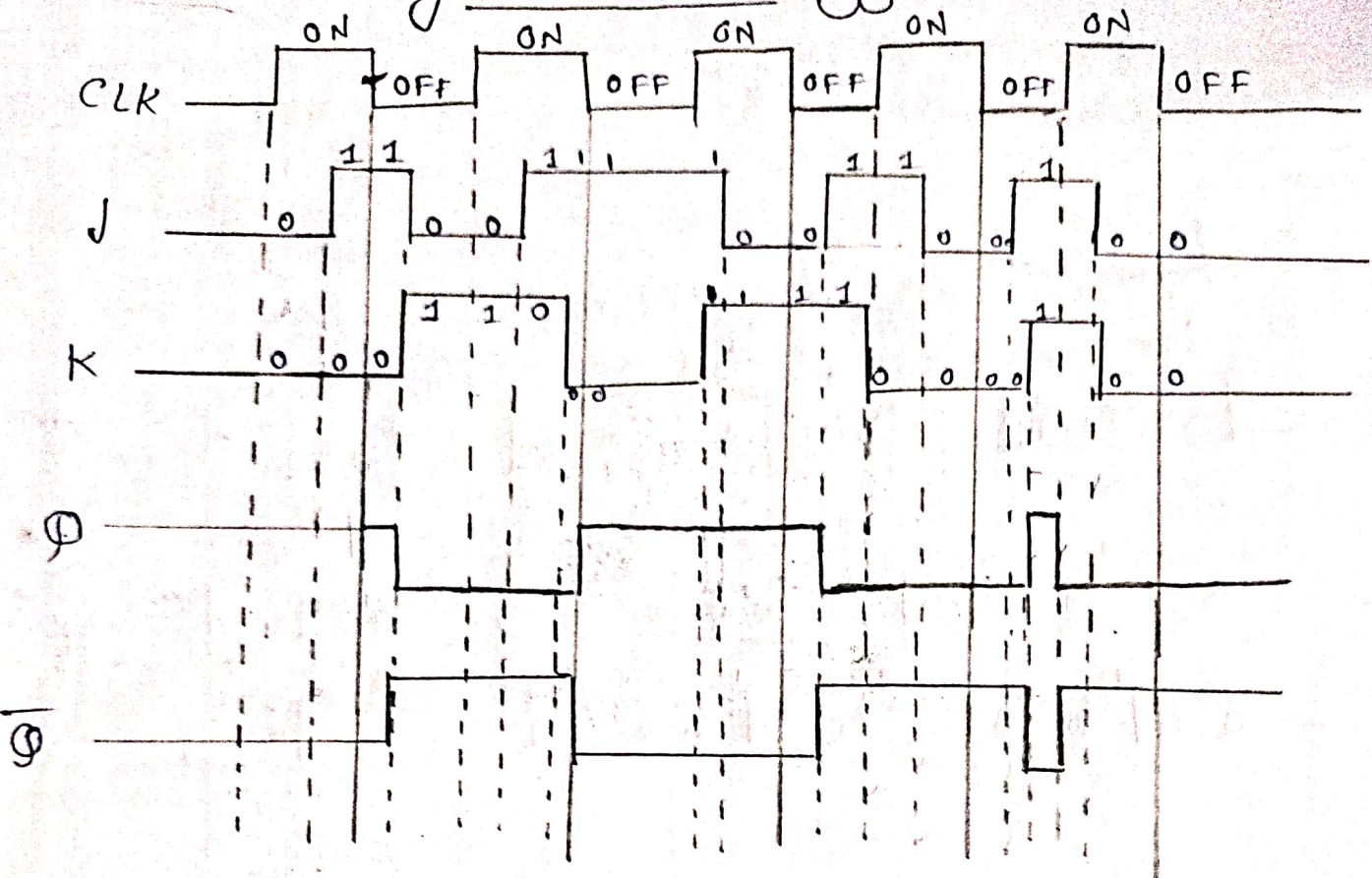


positive level triggered

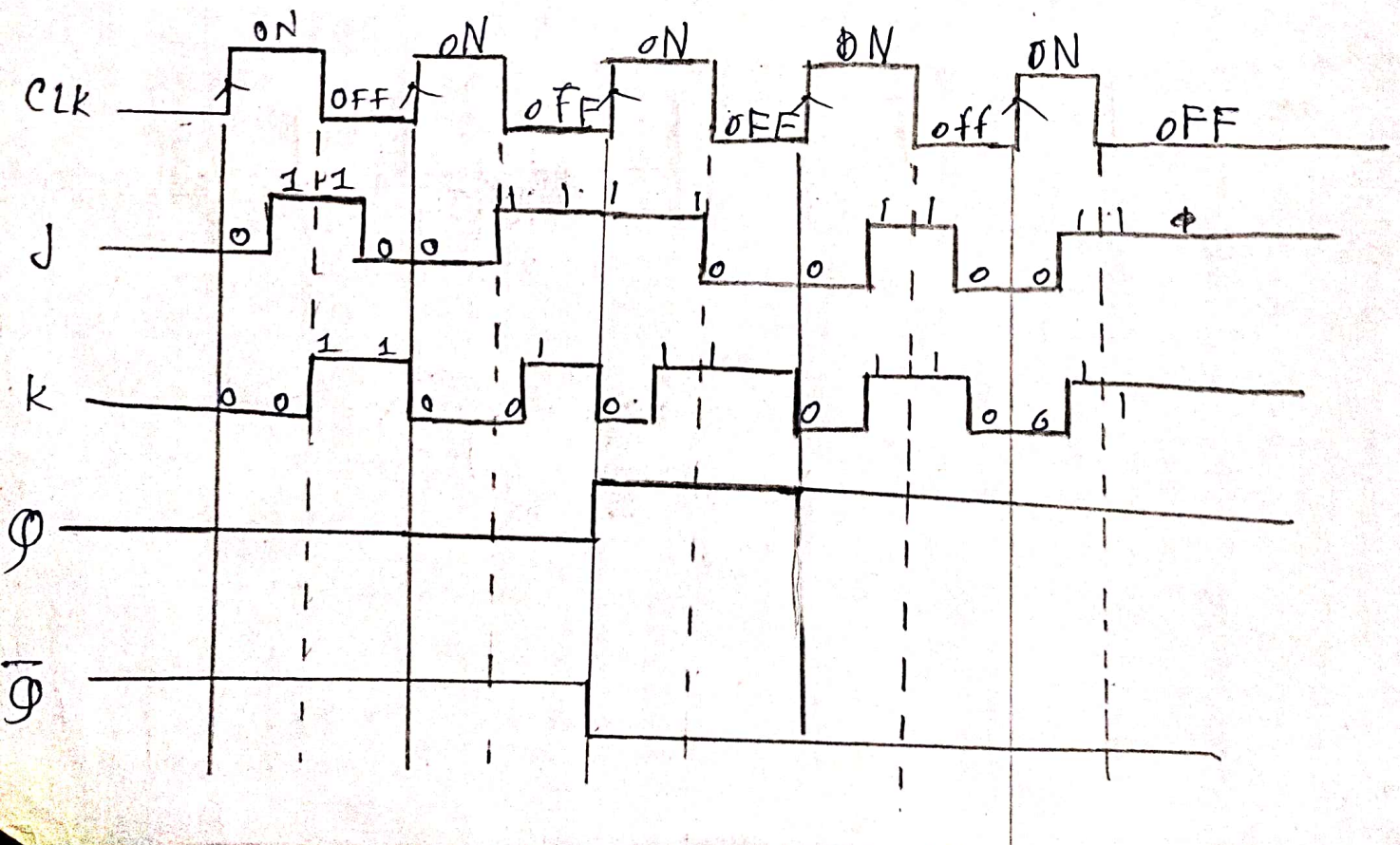



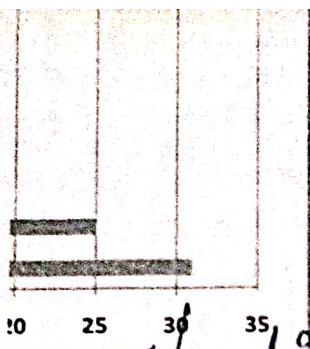


Negative Edge triggered.

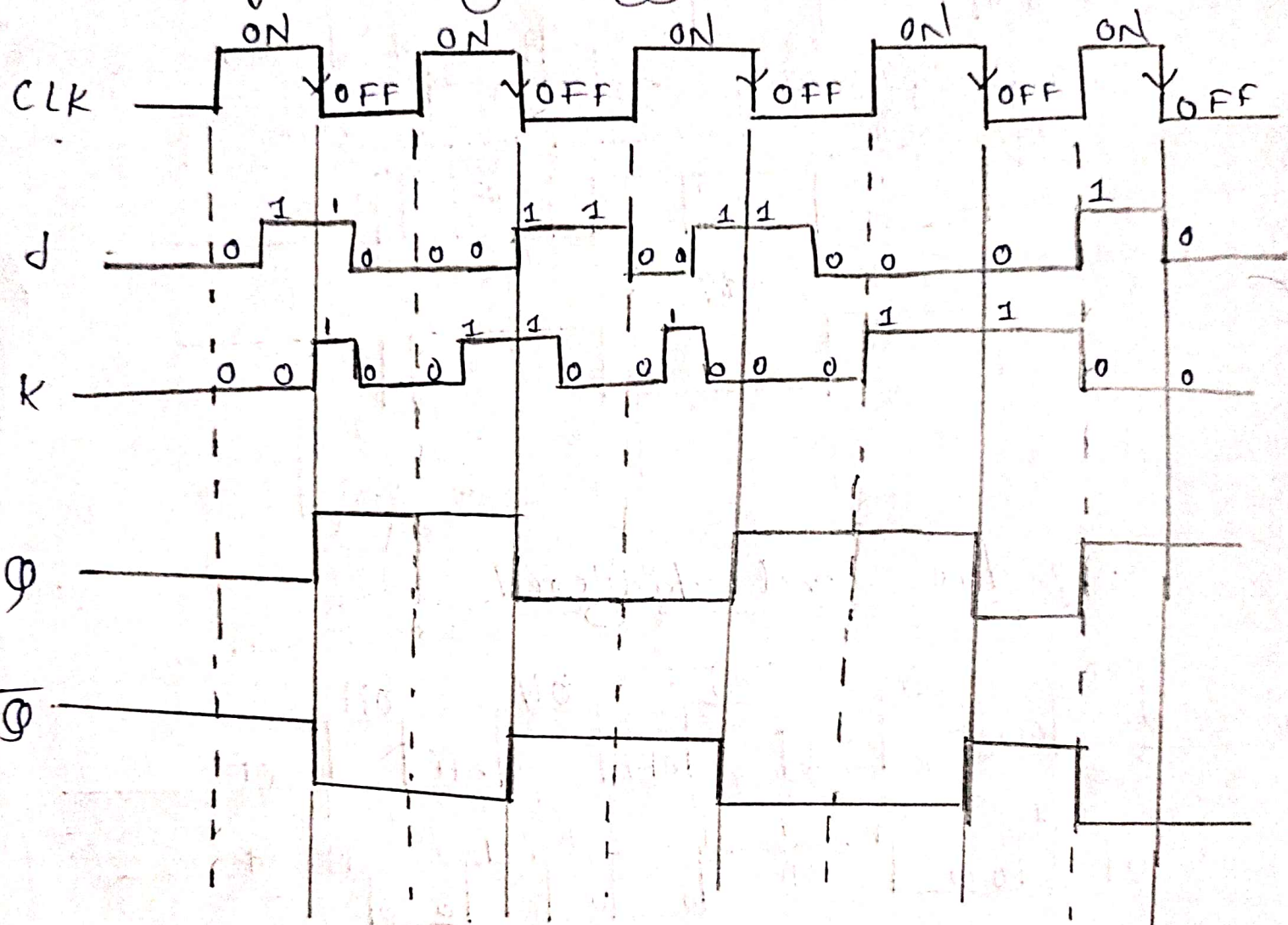

# D - Flip flop

## Block Diagram.

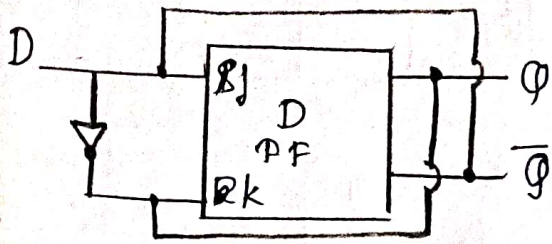

## Truth table.


clk	D	$Q(t+1)$
↓	X	$Q(t)$
↑	0	0
↑	1	1

## Characteristic equation.

$Q(t)$	0	1
0	$Q_0$	$Q_1$
1	$Q_2$	$Q_3$

$$Q(t+1) = D$$

## Logic Diagram

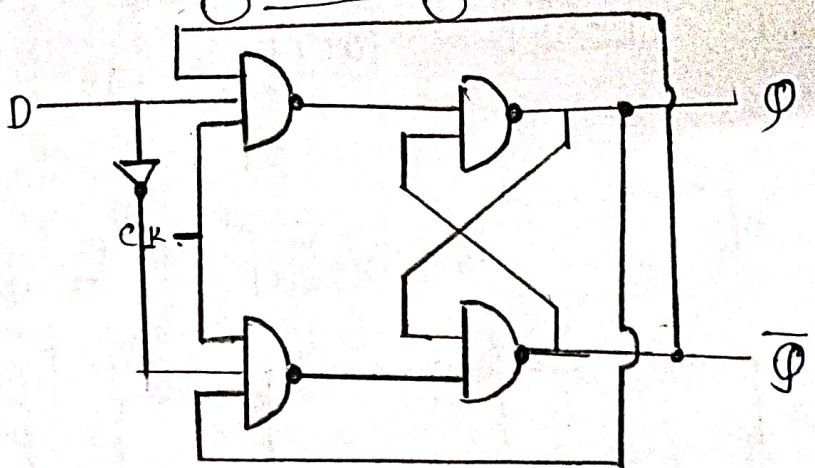

## Characteristic table.


D	$Q(t)$	$Q(t+1)$
0	0	0
0	1	0
1	0	1
1	1	1

## Excitation table.


$Q(t)$	$Q(t+1)$	D
0	0	0
0	1	1
1	0	0
1	1	1



positive level triggered

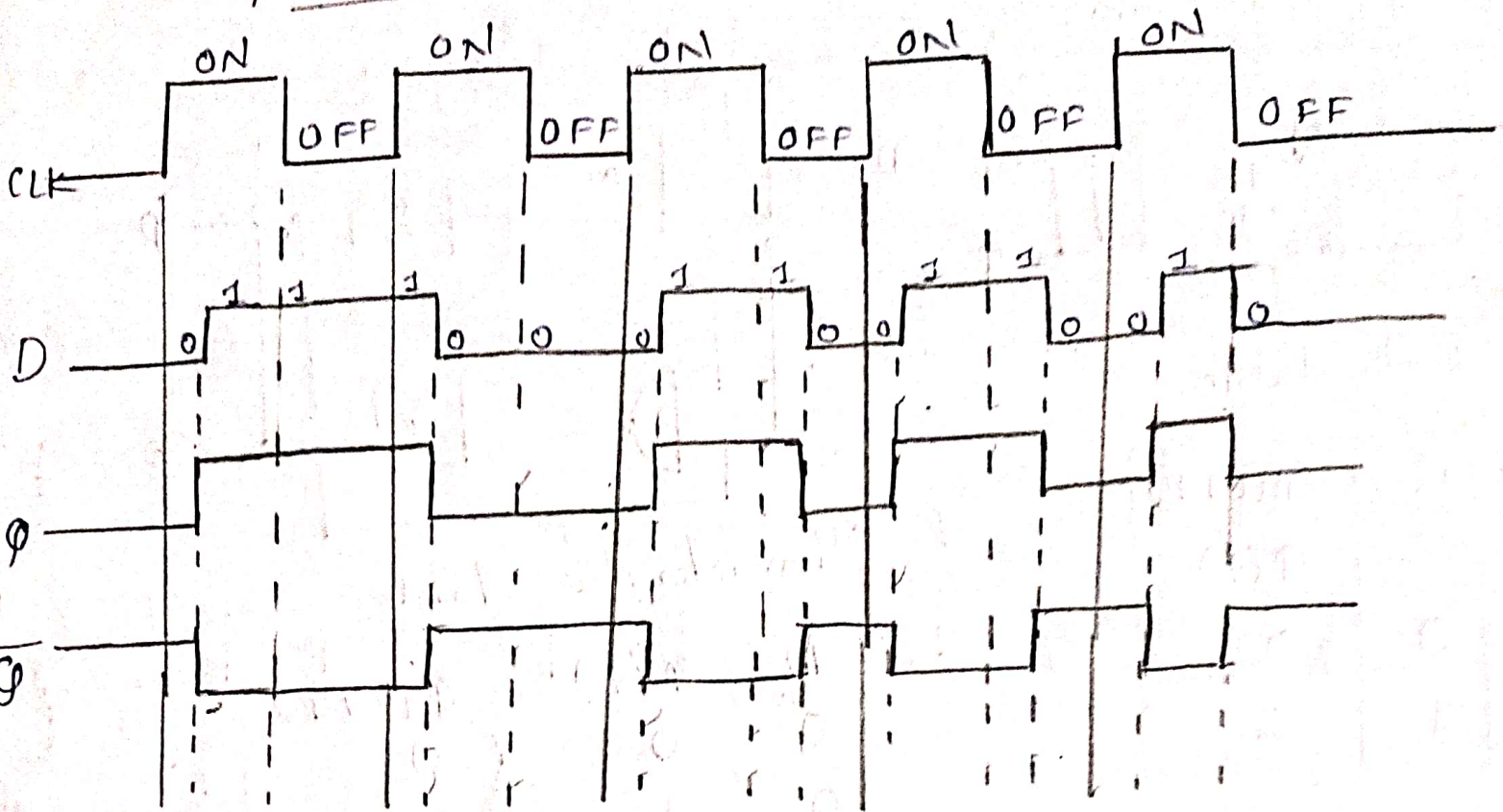


positive edge triggered

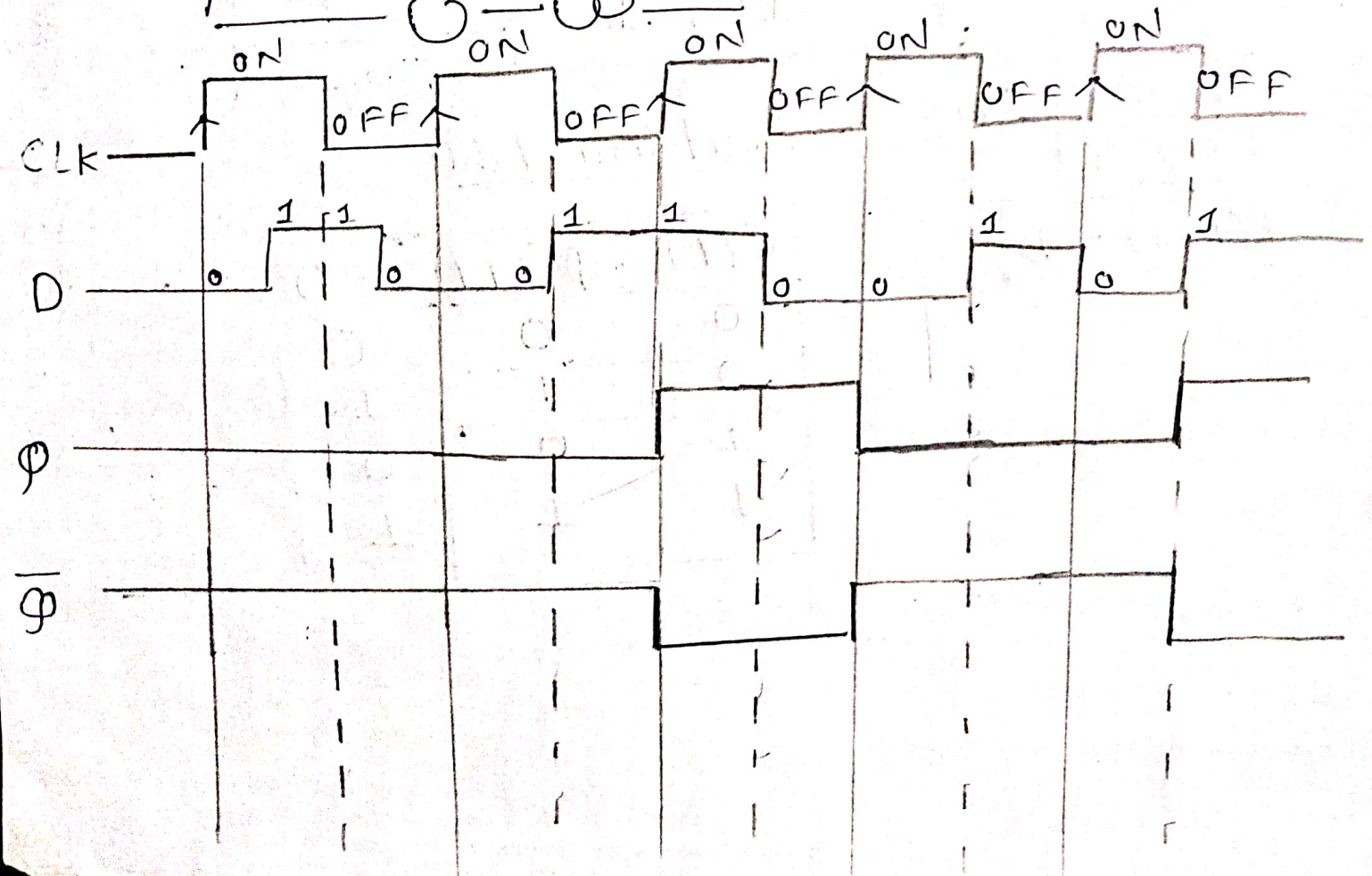


T flip flop

Block Diagram

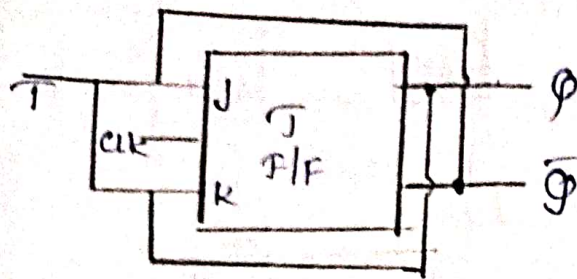

Logic Diagram

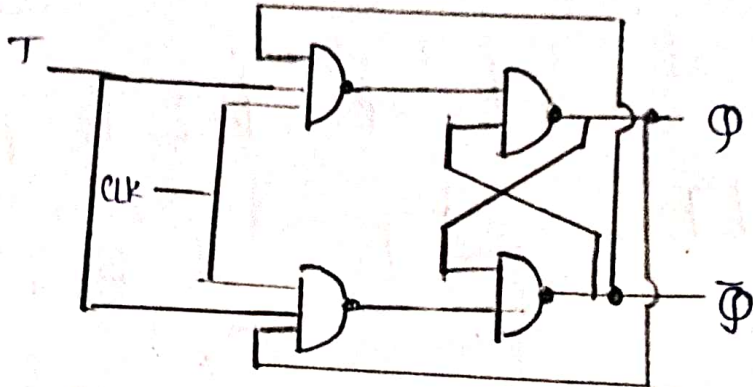

Truth Table

clk	T	$Q(t+1)$
↓	X	$Q(t)$
↑	0	$Q(t)$
↑	1	$\overline{Q(t)}$

Characteristic table

T	$Q(t)$	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

Characteristic equation

T	$Q(t)$	0	1
0	0	0 <sub>0</sub>	1 <sub>1</sub>
1	0	1 <sub>2</sub>	0 <sub>3</sub>

$\overline{Q(t)} \overline{T} Q(t)$  (for cell 1<sub>1</sub>)  
 $T \overline{Q(t)}$  (for cell 1<sub>2</sub>)

$$Q(t+1) = \overline{T} Q(t) + T \overline{Q(t)}$$


Excitation Table

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0



## Waveforms.

positive level triggered.

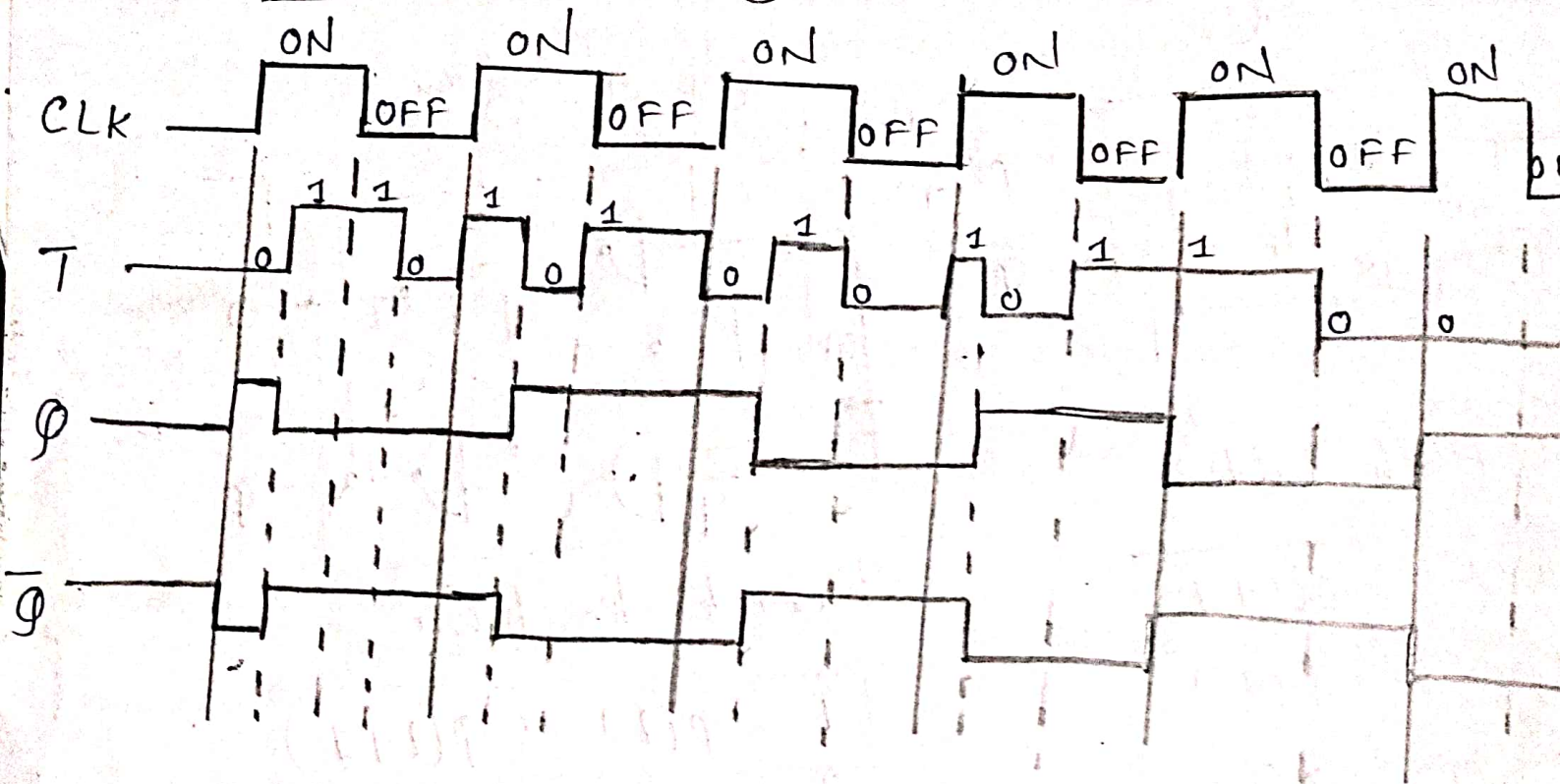

positive edge triggered

