

$\phi$  f/f  $0 \rightarrow 2 \rightarrow 4 \rightarrow 6 \rightarrow 8 \rightarrow 10 \rightarrow 12 \rightarrow 14$   
 counter using JK.

$$\begin{aligned}
 2^n &> 14 \quad \text{where } n=4 \Rightarrow 2^4 = 16 > 14 \rightarrow T \\
 2^3 &= 8 < 14 \rightarrow F \\
 2^4 &= 16 \geq 14 \rightarrow T
 \end{aligned}$$

No. of f/f's = 4 JK flipflop's.

Excitation table for JK flip flop.

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

K-map for J D

$\Phi_D \Phi_C \Phi_B \Phi_A$

	00	01	11	10
00	0 <sub>0</sub>	X <sub>1</sub>	X <sub>3</sub>	0 <sub>2</sub>
01	0 <sub>4</sub>	X <sub>5</sub>	X <sub>7</sub>	0 <sub>6</sub>
11	X <sub>12</sub>	X <sub>13</sub>	X <sub>15</sub>	X <sub>14</sub>
10	X <sub>8</sub>	X <sub>9</sub>	X <sub>11</sub>	X <sub>10</sub>

J D =  $\Phi_B \Phi_C$

K-map for K D

$\Phi_D \Phi_C \Phi_B \Phi_A$

	00	01	11	10
00	X <sub>0</sub>	X <sub>1</sub>	X <sub>3</sub>	X <sub>2</sub>
01	X <sub>4</sub>	X <sub>5</sub>	X <sub>7</sub>	X <sub>6</sub>
11	0 <sub>12</sub>	X <sub>13</sub>	X <sub>15</sub>	1 <sub>14</sub>
10	0 <sub>8</sub>	X <sub>9</sub>	X <sub>11</sub>	0 <sub>10</sub>

K D =  $\Phi_B \Phi_C$

K-map for J C

$\Phi_D \Phi_C \Phi_B \Phi_A$

	00	01	11	10
00	0 <sub>0</sub>	X <sub>1</sub>	X <sub>3</sub>	1 <sub>2</sub>
01	X <sub>4</sub>	X <sub>5</sub>	X <sub>7</sub>	X <sub>6</sub>
11	X <sub>12</sub>	X <sub>13</sub>	X <sub>15</sub>	X <sub>14</sub>
10	0 <sub>8</sub>	X <sub>9</sub>	X <sub>11</sub>	1 <sub>10</sub>

J C =  $\Phi_B$

K-map for K C

$\Phi_D \Phi_C \Phi_B \Phi_A$

	00	01	11	10
00	X <sub>0</sub>	X <sub>1</sub>	X <sub>3</sub>	X <sub>2</sub>
01	0 <sub>4</sub>	X <sub>5</sub>	X <sub>7</sub>	1 <sub>6</sub>
11	1 <sub>12</sub>	X <sub>13</sub>	X <sub>15</sub>	1 <sub>14</sub>
10	X <sub>8</sub>	X <sub>9</sub>	X <sub>11</sub>	X <sub>10</sub>

K C =  $\Phi_B$

K-map for J B

$\Phi_D \Phi_C \Phi_B \Phi_A$

	00	01	11	10
00	1 <sub>0</sub>	X <sub>1</sub>	X <sub>3</sub>	X <sub>2</sub>
01	1 <sub>4</sub>	X <sub>5</sub>	X <sub>7</sub>	X <sub>6</sub>
11	1 <sub>12</sub>	X <sub>13</sub>	X <sub>15</sub>	X <sub>14</sub>
10	1 <sub>8</sub>	X <sub>9</sub>	X <sub>11</sub>	X <sub>10</sub>

J B = 1

K-map for K B

$\Phi_D \Phi_C \Phi_B \Phi_A$

	00	01	11	10
00	X <sub>0</sub>	X <sub>1</sub>	X <sub>3</sub>	1 <sub>2</sub>
01	X <sub>4</sub>	X <sub>5</sub>	X <sub>7</sub>	X <sub>6</sub>
11	X <sub>12</sub>	X <sub>13</sub>	X <sub>15</sub>	1 <sub>14</sub>
10	X <sub>8</sub>	X <sub>9</sub>	X <sub>11</sub>	X <sub>10</sub>

K B = 1

K-map for J A

$\Phi_D \Phi_C \Phi_B \Phi_A$

	00	01	11	10
00	0 <sub>0</sub>	X <sub>1</sub>	X <sub>3</sub>	0 <sub>2</sub>
01	0 <sub>4</sub>	X <sub>5</sub>	X <sub>7</sub>	0 <sub>6</sub>
11	0 <sub>12</sub>	X <sub>13</sub>	X <sub>15</sub>	0 <sub>14</sub>
10	0 <sub>8</sub>	X <sub>9</sub>	X <sub>11</sub>	0 <sub>10</sub>

J A = 0

K-map for K A

$\Phi_D \Phi_C \Phi_B \Phi_A$

	00	01	11	10
00	X <sub>0</sub>	X <sub>1</sub>	X <sub>3</sub>	X <sub>2</sub>
01	X <sub>4</sub>	X <sub>5</sub>	X <sub>7</sub>	X <sub>6</sub>
11	X <sub>12</sub>	X <sub>13</sub>	X <sub>15</sub>	X <sub>14</sub>
10	X <sub>8</sub>	X <sub>9</sub>	X <sub>11</sub>	X <sub>10</sub>


K A = 0




# Excitation table for counter

Present state				Next state											
$Q_0$	$Q_1$	$Q_2$	$Q_3$	$Q_0'$	$Q_1'$	$Q_2'$	$Q_3'$	$J_0$	$K_0$	$J_1$	$K_1$	$J_2$	$K_2$	$J_3$	$K_3$
0	0	0	0	0	0	1	0	0	x	0	x	1	x	0	x
0	0	0	1	x	x	x	x	x	x	x	x	x	x	x	x
0	0	1	0	0	1	0	0	0	x	1	x	x	1	0	x
0	0	1	1	x	x	x	x	x	x	x	x	x	x	x	x
0	1	0	0	0	1	1	0	0	x	x	0	1	x	0	x
0	1	0	1	x	x	x	x	x	x	x	x	x	x	x	x
0	1	1	0	1	0	0	0	1	x	x	1	x	1	0	x
0	1	1	1	x	x	x	x	x	x	x	x	x	x	x	x
1	0	0	0	1	0	1	0	x	0	0	x	1	x	0	x
1	0	0	1	x	x	x	x	x	x	x	x	x	x	x	x
1	0	1	0	1	1	0	0	x	0	1	x	x	1	0	x
1	0	1	1	x	x	x	x	x	x	x	x	x	x	x	x
1	1	0	0	1	1	1	0	x	0	x	0	1	x	0	x
1	1	0	1	x	x	x	x	x	x	x	x	x	x	x	x
1	1	1	0	0	0	0	0	x	1	x	1	x	1	0	x
1	1	1	1	x	x	x	x	x	x	x	x	x	x	x	x

## State Diagram

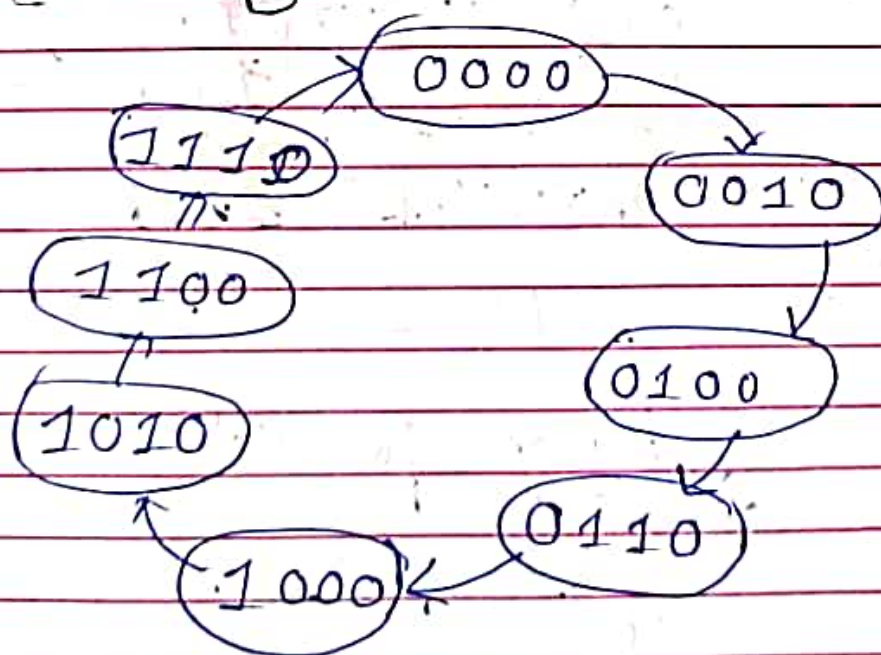

## Logic Circuit

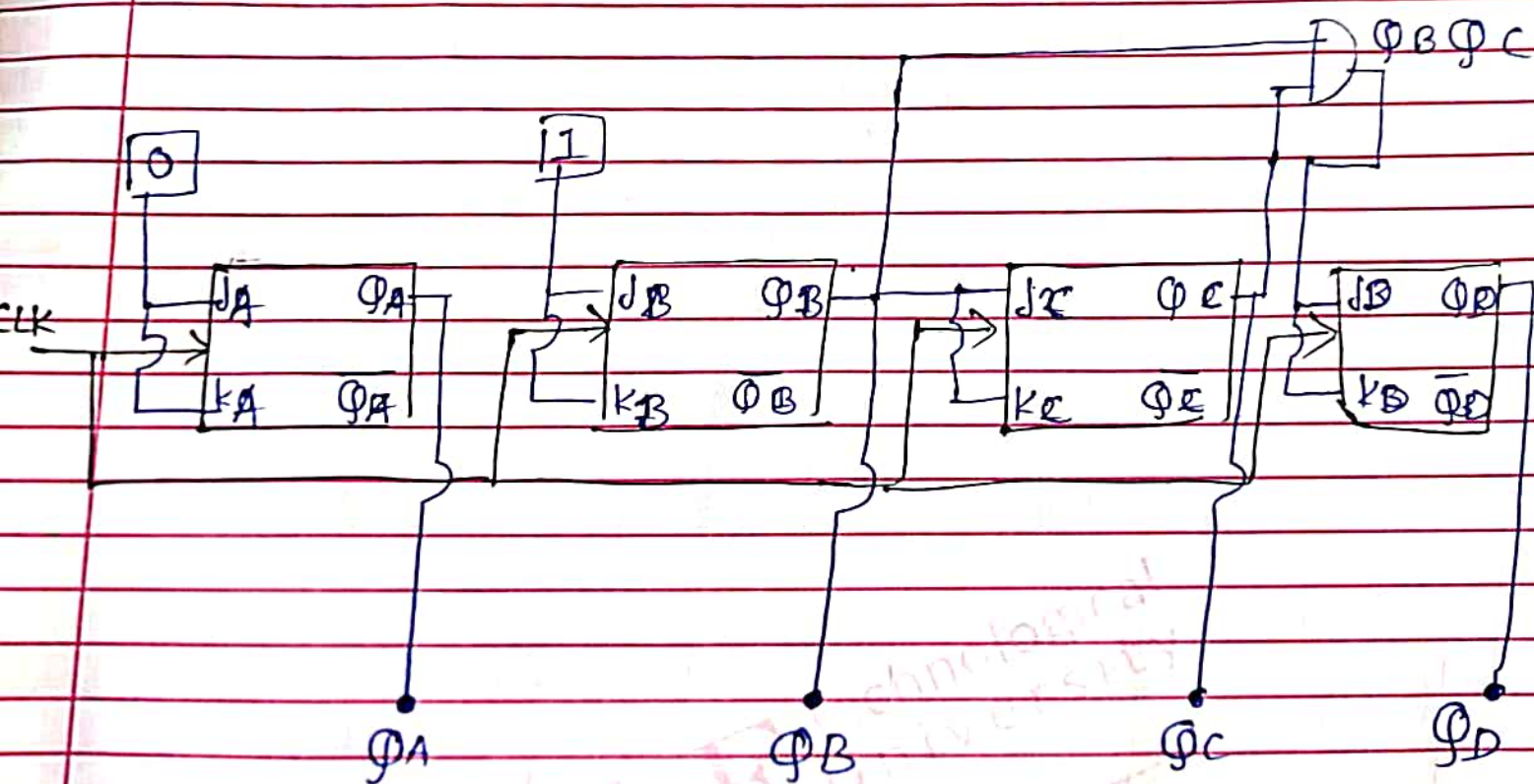



0→2→4→6→8→10→12→14 using JK Flip flop

